

Memory Array

- Typically want an aspect ratio that is not too far from square
- How to divide up the row, column address decoding?


Use an 8K x 32 SRAM = 256 Kb = 2^{18}

$2^{18} = 2^9 \text{ rows} \times 2^9 \text{ columns}$

Row decoder is 9 to 512 decoder

Every 32 (2^5) columns is a 'word', and we only need to decode words. So, column decoder needs to decode 2^4 words, so need a 4 to 16 column decoder.


6-transistor SRAM Cell

 

BR 9/01


6-transistor SRAM Cell

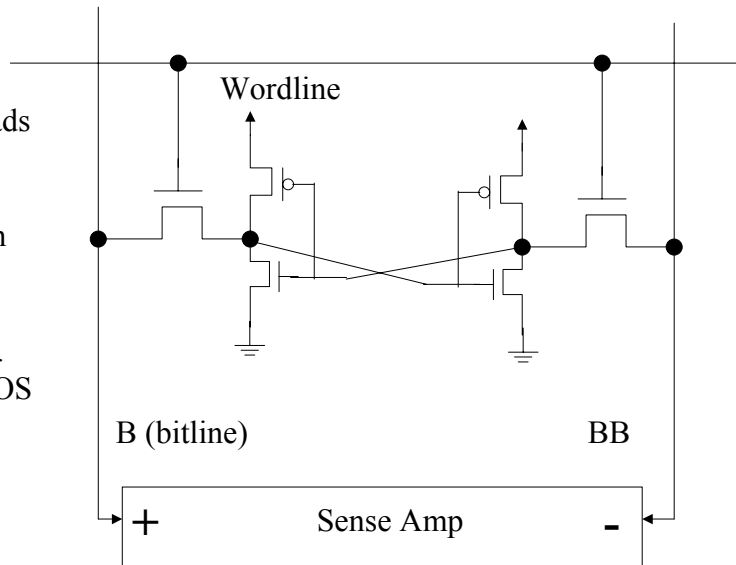PMOS loads
– no static
power
dissipation
except for
leakage,
larger cell.
Want PMOS
small as
possible




BR 9/01

6-transistor SRAM Cell

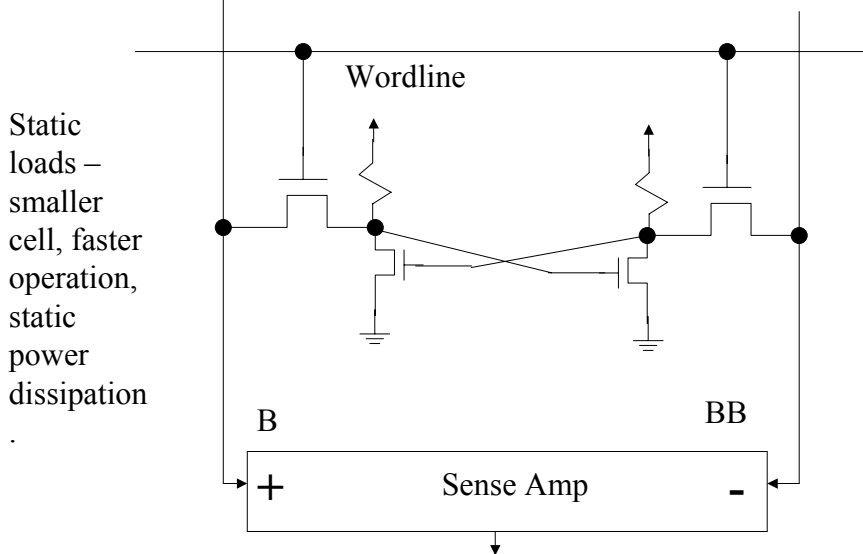



Bit Line vs Word Line

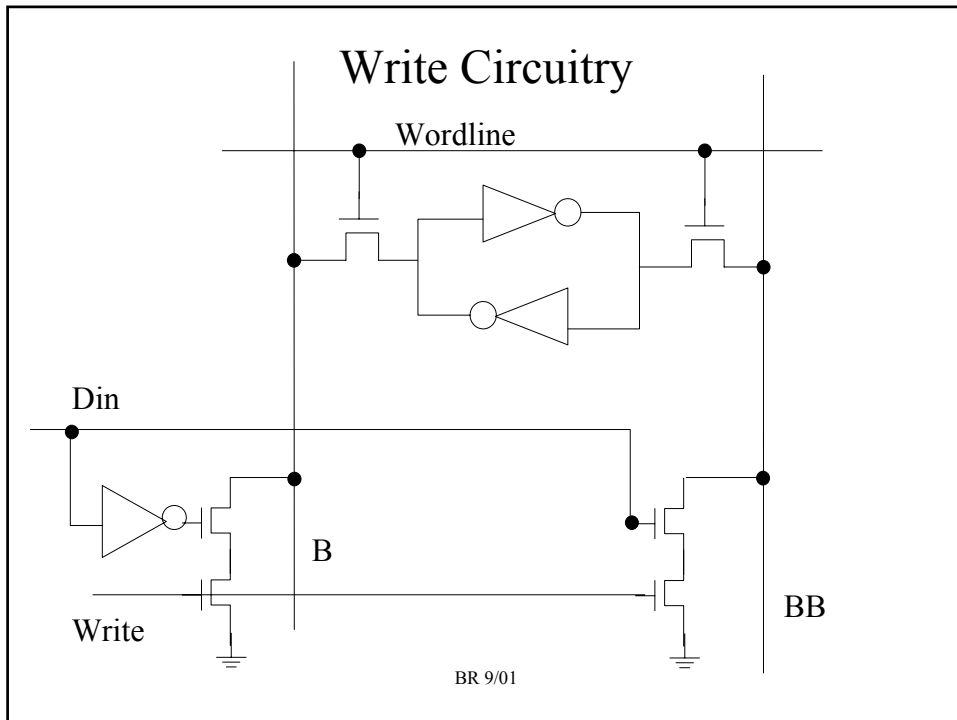- Assertion of word line accesses all cells in a row
 - Not all bits that are read from a row may be used.
 - Loading on word line is high!
- Bit lines connect all cells in a column, only one cell in a column can ever be on at a time
 - Would like to keep bitline swing low in order to preserve power
 - Sense Amp function is to detect bit line change and produce a full '0' or '1' for output latch



Bit Line Biasing

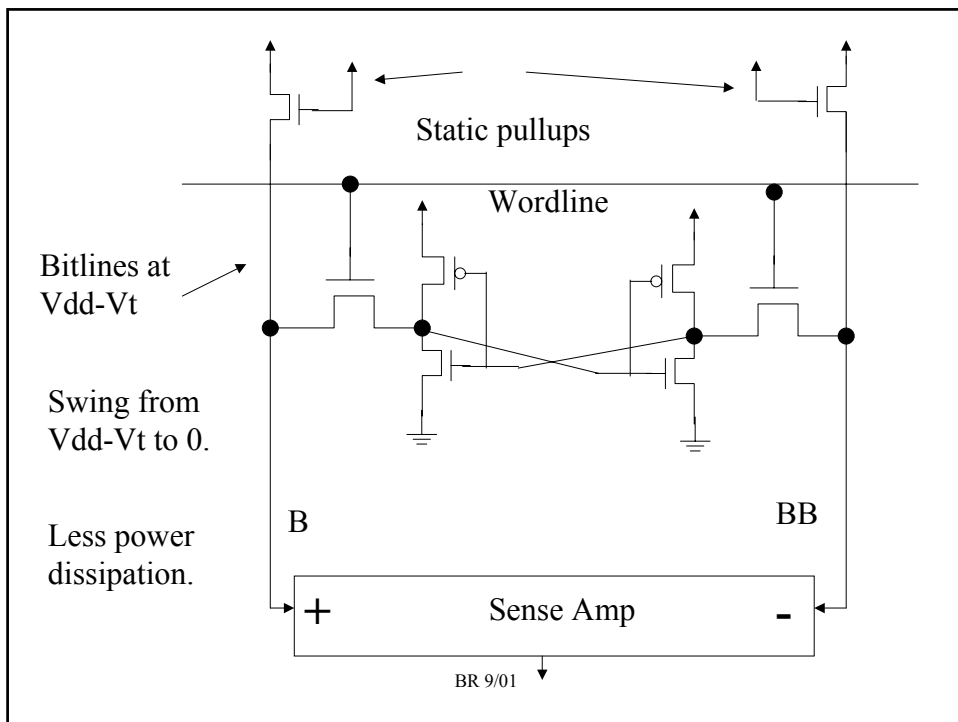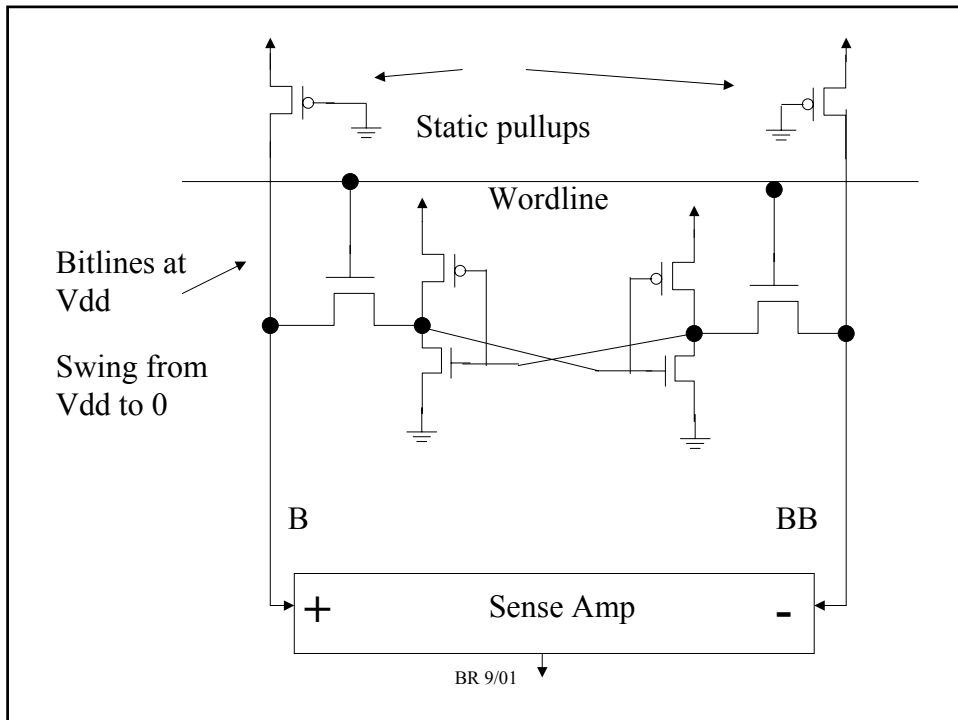
- Bit lines are typically biased somewhere between 0 and Vdd
 - improve speed of cell for reading/writing
 - limit bitline voltage swing for power savings
- Bit line biasing circuit at top of each column
- Bit line biasing circuit can either be static or dynamic (dynamic operation controlled by clock or pulse generated by address line change)



Word Line Kill Approach

- Only turn on word line for a short period of time
- Will allow RAM cell to only drive bit lines for short period, will limit bit-line swing
- Need self timed circuit to 'turn off' word line
- SRAM easy to self-time by including a dummy cell at END of row (last column is column of dummy cells, 1 dummy cell per 16 rows).
 - When signal arrives at dummy column, then all cells in row have been accessed
- Access of dummy cell feeds back to row decoding to turn OFF word line and turn ON sense amp.

BR 9/01

 


BR 9/01

LWL_KILL vs WL_KILL

- Circuit used in L1 Cache of 250 Mhz PowerPC
 - 32 KB divided into 1KB subarrays
 - 1KB subarray 128 rows x 64 columns (8Kb)
- 8 Local Word Line kill lines (1 per 16 rows)
 - Note that LWL_KILL based on bit line output of dummy cell.
 - LWL_KILL turns off decoding for this
- All local word kills are wire or'ed together to form a global word line kill that indicates minimum bit line separation has occurred, so can turn on sense amp.


BR 9/01

Sense Amp (pg 598, Rabaey)

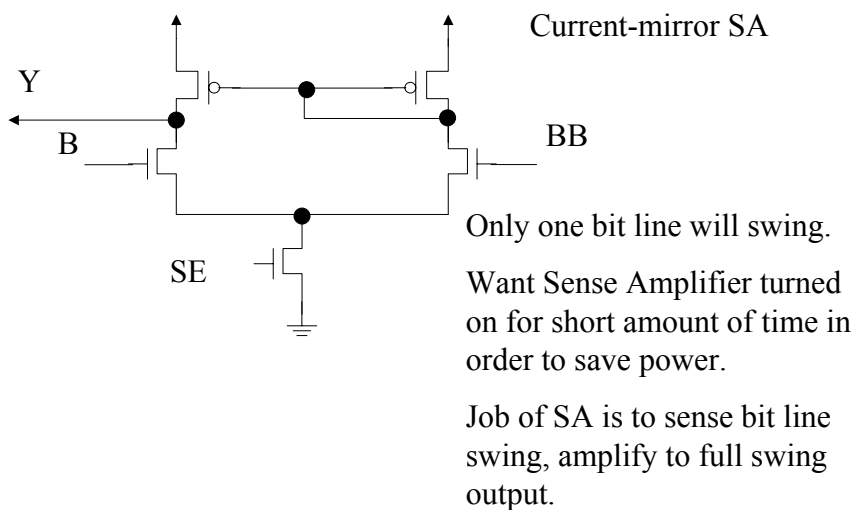


BR 9/01

Sharing Sense Amplifiers

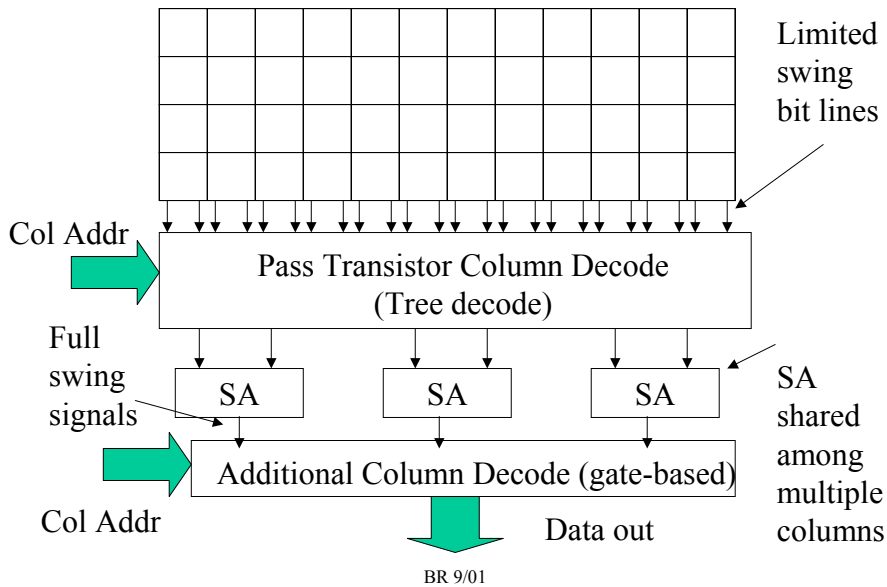

4 to 1 Tree Decoder (pg. 595, Rabaey)

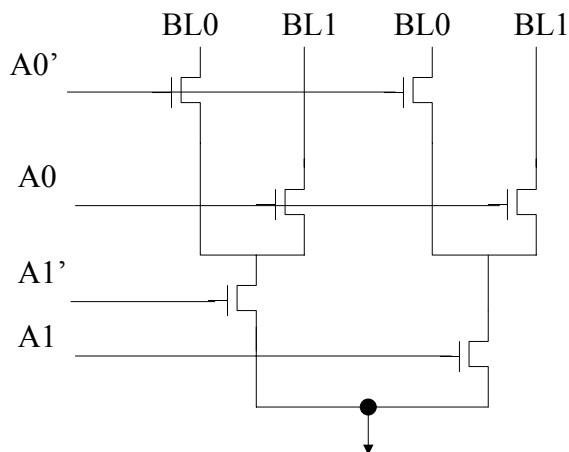

Are able to use nmos-only pass transistors because of limited swing.

Number of pass transistors in series is a concern, but limited swing helps speed.

Improving Speed, Saving Power

Critical path runs through row decode, word line assertion

- Need smaller decoding, less word line capacitance in order to improve speed.
- Break a large array into smaller sub-arrays, and use hierarchical decoding to select a sub array
 - PowerPC 32K x 8 cache broken into 32 blocks, each 1K x 8
 - Cypress 1Mb Dual Port broken into 32 blocks, each 32 K bits ($2^5 \times 2^5 \times 2^{10} = 2^{20}$). Each blocks is 512 rows x 64 columns
 - Mitsubishi SRAM (Rabaey text). 32 blocks of 128K bits (1024 rows x 128 columns)
- Only one sub-array will be activated, saves power!!!!