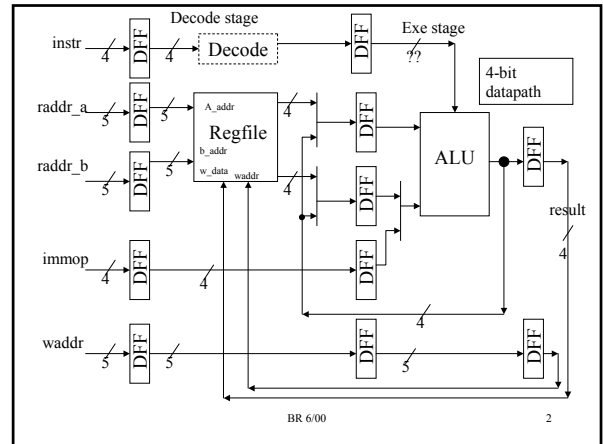


## Simple Pipelined System

- All Spice problems in this homework are to be done for technologies
  - tsmc018.model, Vdd = 2.5 V, default temp
  - all input waveforms should have rise/fall times of 200 ps.
- It is encouraged that you work in teams of two (if you work alone, you must provide me with a reason).
- Will be worth twice that of previous assignments.

BR 6/00

1



## Goal

- Implement a simple pipelined system using static CMOS
- Goal is performance
- Problems you will face
  - Clock network will have a significant load
  - Must generate a gate level netlist from an RTL description
  - Must choose your own cells for this for this implementation.

BR 6/00

3

## Design Constraints

- Create your own Verilog, Spice level gate library for this design
  - Any complex gate design is valid
  - For spice level netlists, use the P\_def and N\_def transistor subcells used in previous labs
  - Other than inverters, no transistor can exceed a width of  $8 \cdot w_{min}$ . For inverters, cannot use anything transistor larger than  $32 \cdot w_{min}$ .
  - No layout – just spice level netlists
  - Can use any DFF design that you can find
  - Might want to consider integrating logic with latches to increase speed
- The register file will be simulated using a Verilog-A model in the spice level netlist.

BR 6/00

4

## Design Constraints (cont.)

- You are free to design the ALU anyway you want to meet the required functionality
  - You cannot move any logic from the EXE stage back into the Decode stage other than doing pre-decoding on the instruction
- You must provide a Verilog gate level netlist that implements the RTL
  - Must be compatible with the current Verilog testbench
- I will provide a Spectre testbench at a later date
  - All inputs, including the clock, will driven by 1X buffers
  - All extra drive will have to be provided by your spice netlist implementation

BR 6/00

5


## Supported Instructions

- Three operand format
  - op rdest, ra, rb      rdest = ra op rb
- Arithmetic: add, sub
- Logic: xor, and, or
- Other: slt, sltu
- Set-Less-Than (slt rdest, ra, rb)
  - Rdest = 1 if ra < rb (signed comparison)
- Set-Less-Than-Unsigned (sltu rdest, ra, rb)
  - Rdest = 1 if ra < rb (unsigned comparison)

BR 6/00

6

### One Possible ALU Structure

 

aluop: Add, Sub, And, Or, Xor

setop: Slt, Sltu, or pass through if not a Set instruction

BR 6/00

7

### Add/Sub/And/Or Cell

 


Diagram from  
Computer  
Architecture  
textbook. Need to  
add XOR.

Operations: AND, OR, ADD, SUB

If SUB, then Carryin LSB = 1, Binvert = 1.

BR 6/00

8

### Overflow Flag Logic

Overflow logic depends on whether doing an addition or subtraction:

if (addition) overflow = (*Amsb* and *Bmsb* and (not *Smsb*)) or  
( (not *Amsb*) and (not *Bmsb*) and *Smsb*)

i.e. For addition, if sign bits of operands are the same, but the result sign bit is different, then OVERFLOW has occurred. *Smsb* is the most significant bit of the result.

If (subtraction) OF = (*Amsb* and (not *Bmsb*) and (not *Smsb*)) or  
(not *Amsb*) and *Bmsb* and *Smsb*)

Note: In all cases, Binvert = 1 for subtraction, Binvert = 0 for add

BR 6/00

9

### Set Logic

SLT, SLTU : output is non-zero if  $A < B$ ; ALU always does a SUB operation, SET logic will output a zero or non zero value based on flags.

if SLT (signed comparison) then

Let *Nf* = sign bit of result, OF = overflow

Result (LSB) = ( (not OF) and *Nf*) or (OF and (not *Nf*))

Result other bits = 0.

If SLTU (unsigned comparison) then

Result (LSB) = not(CarryFlag)

Result other bits = 0.

Note that a Set operation always produces as a result either '1' ('0001') or '0' ('0000').

BR 6/00

10

### Verilog RTL, Testbench

- In distribution, the directory `./modelsim/src/alu_rtl` contains the verilog files
  - `alu.v` - RTL for pipelined system
  - `tb_alu.v` - testbench for `alu.v`
- To place modelsim on path do 'swsetup modelsim'
- To compile files do
  - `cd ./modelsim/src/alu_rtl`
  - `gmake -f alu_rtl/Makefile`
- To run simulation:
  - `qhsim -lib alu_rtl tb_alu -c -do "run 20 us;quit"`

BR 6/00

11

### Verilog Testbench

- The Verilog testbench file (`tb_alu.v`) reads a file called 'prog.obj' that contains the object code for the program to be executed.
- A perl script (`assemble.pl`) is used to assemble a program.
  - `assemble.pl add_prog.asm` will produce an object file called `add_prog.obj`
  - You should either link or copy your object file to 'prog.obj'.
- The perl script is `./modelsim/src/assemble.pl`
- Testbench provides inputs on rising clock edge.

BR 6/00

12

## A Sample Program

```
# comment line
add r1,r0,1 # r1 = 1
add r2,r0,2 # r2 = 2
add r3,r1,r2 # r3 = 3, activate bypass B
add r3,r3,r1 # r3 = 3+1 = 4, activate bypass A
sub r4,r3,r3 # r4 = 0
add r7,r3,-7 # r7 = 4-7 = -3 (0x13)
```

dest      srcA, must be a register  
srcB, can be register or 4-bit signed immediate

Registers: r0-r31, r0 is always '0'.

BR 6/00

13

## Object Code file produced by 'assemble.pl'

```
// add r1,r0,1 # r1 = 1
1_011_00001_00000_00000_0001
// add r2,r0,2 # r2 = 2
1_011_00010_00000_00000_0010
// add r3,r1,r2 # r3 = 3, activate bypass B
0_011_00011_00001_00010_0000
// add r3,r3,r1 # r3 = 3+1 = 4, activate bypass A
0_011_00011_00011_00001_0000
// sub r4,r3,r3 # r4 = 0
0_100_00100_00011_00011_0000
// add r7,r3,-7 # r7 = 4-7 = -3 (0x13)
1_011_00111_00011_00000_1001
```

Must copy this file to prog.obj to be read by *tb\_alu.v*

BR 6/00

14

## Object Code format

```
// add r7,r3,-7 # r7 = 4-7 = -3 (0x13)
1_011_00111_00011_00000_1001
```

Ibit='1' if  
srcB was  
immediate

Instruction  
opcode

Dest reg

srcA  
reg

srcB reg,  
0 if  
immediate  
used.

Immediate  
field

BR 6/00

15

```
module tb_alu;
wire [3:0] result, instr;
wire [4:0] waddr,raddr_a,raddr_b;
wire [3:0] immop;
reg clk;

reg [(1+3+5+5+4)-1:0] program[0:100];
integer pc,i;

assign {instr[3],instr[2:0],waddr,raddr_a,raddr_b,immop} = program[pc];
alu alu0 (result,instr,raddr_a,raddr_b,waddr,immop,clk);
initial begin
    clk = 0; pc = 0;
    for (i=0;i<100;i=i+1) program[i] = 0;
    $readmemb("prog.obj",program);
    /* run clock cycles */
    for (i=0;i<100;i=i+1)
    begin
        #100 clk = 1;
        #100 clk = 0;
        pc = pc +1;
    end
end
endmodule
```

*tb\_alu.v*

Declare program  
memory array

Instantiate  
ALU

Read 'prog.obj'  
file.

Run 100 clock cycles

BR 6/00

16

## *alu.v*


- Contains modules for the register file and alu (the 'alu' module contains everything except the register file)
- Register file module prints to screen anytime a write to register other than 'r0' occurs.
- Module *alu.v* contains the RTL for the functionality of the system
  - You could just synthesize this directly to a gate level netlist using a simple standard cell library, but the resulting logic would not be that fast
  - The block diagram shown earlier corresponds to the RTL description

BR 6/00

17
 
## Register File (32 x 4)

Register file is two read ports, one write port.  
32 locations, 4 bits/location



BR 6/00

18

## Register File in *alu.v*

```
module regfile(a_data,b_data,raddr_a,raddr_b,waddr, w_data, wbit,clk);
output [3:0] a_data,b_data;
input [4:0] raddr_a,raddr_b,waddr;
input [3:0] w_data;
input wbit,clk;

integer j;
/* declare register file */
reg [3:0] rf[31:0];
initial rf[0] = 0;

always @(wbit or clk or waddr or w_data)
begin
    if (clk & wbit) begin
        if (waddr != 0) rf[waddr] = w_data;
    end
end

assign #1 a_data = rf[raddr_a];
assign #1 b_data = rf[raddr_b];
endmodule
```

Do a write when  $\text{clk}=1$  and  $\text{wbit}=1$ . In *alu*, the  $\text{wbit}$  is always '1', but could change later.

Two read ports

BR 6/00

19

## Module *alu* in *alu.v*

```
module alu (result,instr,raddr_a,raddr_b,waddr,immop,clk);
`define XOR_OP 0
`define OR_OP 1
`define AND_OP 2
`define ADD_OP 3
`define SUB_OP 4
`define SLT_OP 5
`define SLTU_OP 6

output [3:0] result;
input [3:0] instr;
input [4:0] raddr_a,raddr_b,waddr;
input [3:0] immop;
input clk;
```

Opcodes: cannot change!

Interface to system, cannot change this!!!

BR 6/00

20

## *alu.v* (cont).

```
/* decode stage registers*/
always @(posedge clk) id_instr = #1 instr;
always @(posedge clk) id_raddr_a = #1 raddr_a;
always @(posedge clk) id_raddr_b = #1 raddr_b;
always @(posedge clk) id_waddr = #1 waddr;
always @(posedge clk) id_immop = #1 immop;
```

Unit delay

Statements like this simply represent a set of DFFs where the input is the right hand side, the output is the left hand side.

BR 6/00

21

## Bypass Paths in Decode Stage

```
always @(posedge clk)
    if (id_raddr_a == exe_waddr) exe_a = #1 exe_result;
    else exe_a = #1 rf_a;
```

Muxes in front of DFFs

```
always @(posedge clk)
    if (id_raddr_b == exe_waddr) exe_b = #1 exe_result;
    else exe_b = #1 rf_b;
```

If destination of previous instruction is equal to source of current instruction, use value from execute stage since it has not been written to register file yet!!!

```
add r2,r0,2 # r2 = 2
add r3,r1,r2 # r3 = 3, activate bypass B
```

BR 6/00

22

## *alu.v* (cont).

```
/* alu, 1st stage */
always @(exe_instr or exe_b or exe_immop)
begin
    if (exe_instr[3]) exe_op_b = exe_immop;
    else exe_op_b = exe_b;
end

always @(exe_instr or exe_a or exe_op_b)
begin
    case (exe_instr[2:0])
        `XOR_OP: exe_result_a = exe_a ^ exe_op_b;
        `OR_OP:  exe_result_a = exe_a | exe_op_b;
        `AND_OP: exe_result_a = exe_a & exe_op_b;
        `ADD_OP: exe_result_a = exe_a + exe_op_b;
        `SUB_OP: exe_result_a = exe_a + ~exe_op_b + 1;
        `SLT_OP: exe_result_a = exe_a + ~exe_op_b + 1;
        `SLTU_OP: exe_result_a = exe_a + ~exe_op_b + 1;
        default: exe_result_a = exe_a;
    endcase
end
```

Combinational logic blocks.

2/1 mux for immediate operand.

Subtraction via 2's complement

ALU comb logic.

BR 6/00

23

## Transforming RTL To Gate Level Netlist

- One approach : could write a Synopsys .lib file for your library and just use synthesis to do transformation
  - Use dummy delays since no time to do characterization
  - Use simple gates like NANDs, NORs
  - Result would work but would be slow
- Another approach: look at required logic at the gate level, and design complex gates to reduce the register-to-register delay time since that will define the maximum clock frequency
  - Write Verilog gate level netlist manually (not that hard for a 4-bit ALU).
  - Execute stage will be the limiting stage so optimize this stage
  - You CANNOT move logic from the execute to the decode stage.

BR 6/00

24

## Writing Gate-level Verilog Modules

- The file `./sample_files/libcells.v` has some sample module definitions for common library functions like nands, nors, xors, etc.
- When writing your gate level modules, do the following:
  - Use either UPPER case or LOWER case for all terminal/module names
  - Do NOT use mixed case
  - I would suggest using lowercase for everything (more readable).
  - Verilog is case sensitive
  - Use unit delays for gate level modules

BR 6/00

25

## A Sample Gate Level Module: Full Adder

```
module FA (SUM,CO, A, B, CI);
  output SUM;
  output CO;
  input A;
  input B;
  input CI;
  xor #2 IO (SUM, A, B, CI);
  and I1 (N1,A, B);
  and I2 (N2,A, CI);
  and I3 (N3,CI, B);
  or #2 I4 (CO,N1,N2,N3);
endmodule
```

Port declarations

Verilog primitive gate

Instance name

Pinlist – for primitives, first pin is output followed by inputs.

Output gate delay – 2 time units.

BR 6/00

26

## A DFF

```
module DFF (Q, CLK, D);
  output Q;
  reg Q;
  input D, CLK;

  initial begin
    Q=0;
  end
  always @(posedge CLK)
    Q = #1 D;
endmodule
```

Triggered on positive clock edge

BR 6/00

27

## Hierarchical Gate-level Verilog

```
module XNOR8G (Y,A,B);
  output [7:0] Y;
  input [7:0] A,B;

  XNOR2X1 I0 (Y[0],A[0],B[0]);
  XNOR2X1 I1 (Y[1],A[1],B[1]);
  XNOR2X1 I2 (Y[2],A[2],B[2]);
  XNOR2X1 I3 (Y[3],A[3],B[3]);
  XNOR2X1 I4 (Y[4],A[4],B[4]);
  XNOR2X1 I5 (Y[5],A[5],B[5]);
  XNOR2X1 I6 (Y[6],A[6],B[6]);
  XNOR2X1 I7 (Y[7],A[7],B[7]);
endmodule
```

A module that instantiates 8 XNOR gates.

Previously declared module.

BR 6/00

28

## Due Dates

- Completed Spice Simulation are due on October 3<sup>rd</sup> (two weeks from today).
- Verilog Gate level simulation due on Thursday Sept 26<sup>th</sup> (this does not have to be the final gate level netlist, just a progress check).
  - Expect two files: `libcells.v` that has gate level modules and `alu.v` that is gate level netlist and register file module (do not change the register file module)

BR 6/00

29

## Rankings

- I will rank designs by achievable clock frequency
  - Spectre testbench will be provided by Thursday, Sept 26<sup>th</sup>.
- Upper 1/3 of class will get 25 points added to any test grade.
- Middle 1/3 will get 12 pts added to any test grade.
- Bottom 1/3 will get no extra points.

BR 6/00

30