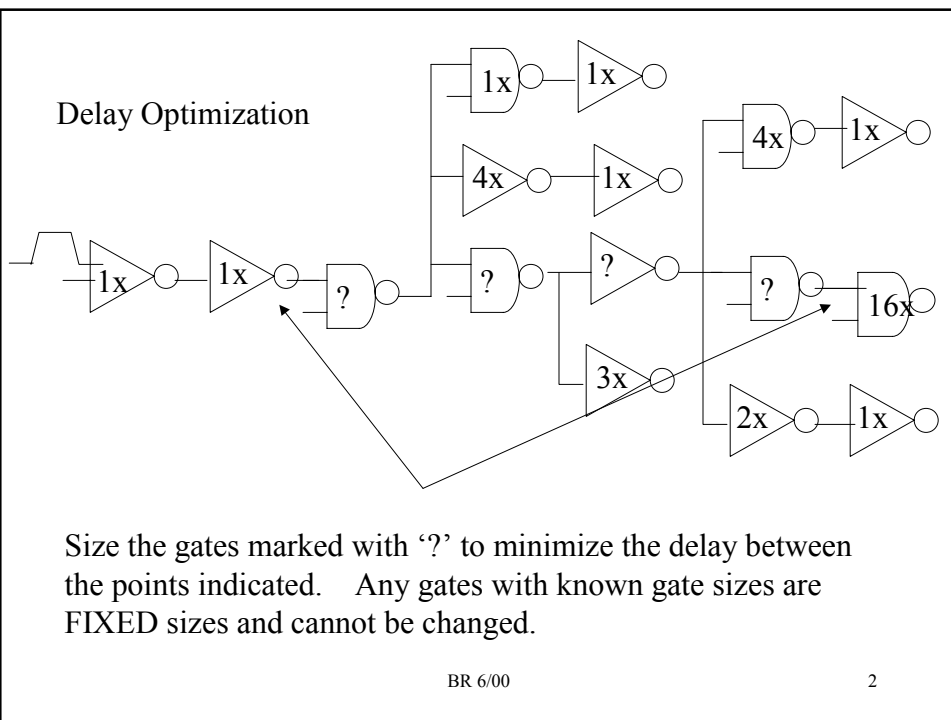


# Delay Optimization Homework

- All Spice problems in this homework are to be done for technologies and conditions
  - tsmc\_0\_35.model, tsmc\_0\_18.model (actually, only one technology will be done by each student, more on this later)
  - Vdd = 3.3 V, default temp
  - all input waveforms should have rise/fall times of 100 ps.

BR 6/00

1



## Details

- If the last digit of your student ID modulo 4 is:
  - 0, use 1.4/1 for your 1X inverter, 0.18 TSMC technology
  - 1, use 2/1 for your 1X inverter, 0.18 TSMC technology
  - 2, use 1.4/1 for your 1X inverter, 0.35 TSMC technology
  - 3, use 2/1 for your 1X inverter, 0.35 TSMC technology
- Scale your 2-input NAND based upon your 1X inverter
  - Use appropriate GEO parameters in your NAND model
- When optimizing the delay, optimize only for TPHL
  - will assume that TPLH will be ok
  - this should reduce the simulation workload
- Assume that you only have gate sizes of 1x to 6x available in 0.5x steps.

## Part #1: Tilos Optimization

- Use the Tilos algorithm to optimize the gate sizes in 0.5X steps.
  - Increase gate sizes by 0.5X during simulation
- All the gates marked with ‘?’ are available for sizing.
- Once the final gate sizes have been chosen, record both TPLH and TPHL through the optimized path.

## Part #2: Logical Effort Optimization

- Use the logical effort approach to optimize the path
  - You will need to use transistor widths to represent load since different gates are being used
- Measure  $\tau$ ,  $P_{inv}$  as specified via Method #2 (see notes) for a 1X inverter.
- Instead of using a computed 'g' value for the *nand2*, measure the 'g' value for a *nand2* as specified in the notes.
- Also measure  $P_{nand2}$  for a 1X sized *nand2*.
- Use these parameters to optimize the gate sizes
  - The off path loads are fixed, so you will have to choose the gate sizes via iteration
  - Convert the final sizes that you get into the nearest .5X gate size (I do not want to see a gate size specified as 2.68X - round to the nearest 0.5X, or 2.5X in this case).
- Measure both TPLH, TPHL once the gate sizes have been chosen.

BR 6/00

5

## Report

- Compare the resulting path delays, gate sizes as optimized in Parts #1, Parts #2
  - Comment upon your results
- Document all of your calculations/measurements as carefully as possible and present the data in a professional manner

BR 6/00

6