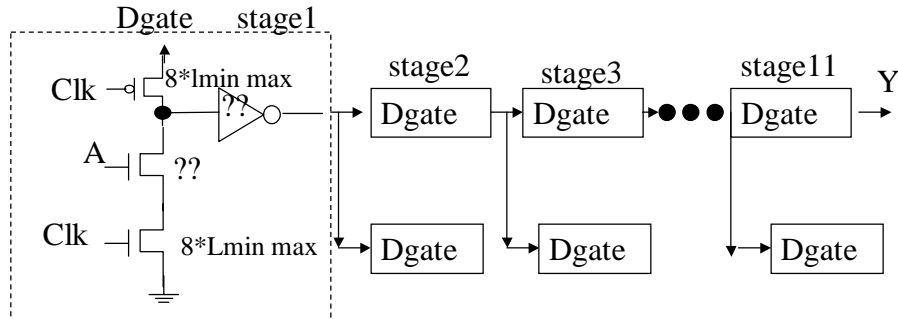


## Problem #1: Domino Logic Sizing



For the 11 stage circuit above, size via simulation the output inverter, and the NMOS pulldown of the DGATE such that the A to Y average delay is within 10% of the minimum delay with the lowest dynamic power consumption. You must not exceed the maximum sizes shown on the precharge/eval transistors. Your clock can be any duty cycle you wish. Note that all DGates are the same size. Use 100 ps rise/fall times on both A, Clk signals. Use Leda 0.25u, Vdd = 2.5. (note: Lmin = .25u).

BR 6/00


1

## Solution to #1

A caveat: there are probably multiple solutions that meet the criteria.

First, what to size?

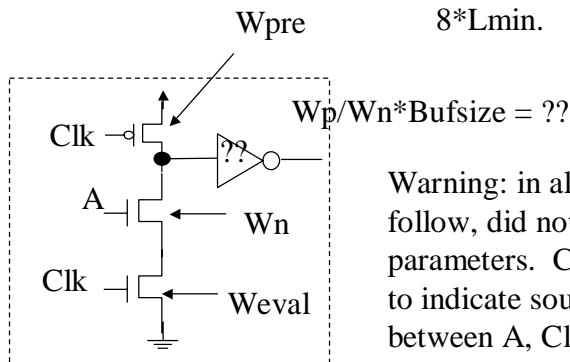The Wpre and Weval could be given maximum sizes of  $8 \cdot L_{min}$ .



Warning: in all simulations that follow, did not use any GEO parameters. Could have used GEO to indicate source/drain sharing between A, Clk n-transistors.

BR 6/00

2

### Try some extremes

pre=8	eval=8			
	Skewed, N=4			
	Eval time	Eval/stg	pre	clk per
Bufsize				
2	1471	134	257	1729
2.5	1438	131	264	1702
3	1418	129	265	1683
3.5	1416	129	267	1683
4	1428	130	265	1693

Large Weval,  
Wpre, Wn.  
High Skew  
output ( $2/.5 * \text{Bufsize}$ )

pre=1	eval=1			
	Skewed, N=1			
	Eval time	Eval/stg	pre	clk per
Bufsize				
2	1261	115	326	1587
2.5	1328	120	355	1682

Min Weval,  
Wpre, Wn.  
High skew  
output ( $2/.5 * \text{Bufsize}$ )

BR 6/00

3

### Small Sizes worked better.

Start at low end, begin increasing sizes of Eval, Pre, and Wn.

Pre  $\uparrow$  would Precharge Time  $\downarrow$ , Eval Time  $\uparrow$

Eval  $\uparrow$  would Precharge Time  $\uparrow$ , Eval Time  $\downarrow$

Since eval time decreases are summed over number of stages, better to decrease Eval time at expense of precharge time.

Eventually found good solution to be:

pre=2	eval=8			
	Skewed, N=1			
	Eval time	Eval/stg	pre	clk per
Bufsize				
2	1222	111	294	1516
2.5	1273	116	319	1592

Weval = 8  
Wpre = 2,  
Wn = 1  
High skew  
output ( $2/.5 * 2$ )

BR 6/00

4

## Adjust Skew

Was using a buffer sized as  $W_p/W_n = 4/1$  (high skew)

Looked at changing skew in both directions to see if this would improve delay.

Found that  $W_p/W_n = 3/1$  gave minimum delay.

pre=2	eval=8			
	Skew 3/1, N=1			
	Eval time	Eval/stg	pre	clk per
Bufsize				
2	1232	112	273	1504
2.5	1259	115	289	1548

Weval = 8  
 $W_{pre} = 2$ ,  
 $W_n = 1$   
 Slightly high  
 skew output  
 (3/1)

BR 6/00

5

## Reduce power

Min. Delay was approximately 1500 ps.

+10% delay = 1650 ps. Go to minimum size with no-skew output, adjust from there.

			Pwr in uW		Tot. Pwr	%diff
Wpre=2, Weval=8	Clk Per.	%diff	Vdd	Clk		
Wn=1, Buff=3/1	1504		198	14	212	
Wpre=1, Weval=1						
Wn=1, Buff=2/1	1286	3.0%	135	3.6	138.6	-34.6%
Wpre=1, Weval=1						
Wn=1, Buff=1.5/1	1586	5.5%	124	3.5	127.5	-39.9%
Wpre=1, Weval=1						
Wn=1, Buff=1/1	1709	13.6%	113	3.5	116.5	-45.0%

Saved approx 40% in power at cost of 5.5% in delay.

BR 6/00

6

## Problem #2

Refer to problem #21, Chapter 4 in the Rabaey textbook.  
Scale the transistor sizes to the Leda 0.25u , use 2.5 V, and do parts a, b, c of the problem.

Use the GEO parameter on your MOSFETs to indicate source/drain diffusion sharing where applicable. Draw a stick diagram of the layout to support your diffusion sharing assumptions. Assume Gate1, Gate2 are separate layout blocks.


BR 6/00

7
 
## Circuit Function

$$F = A0 B0 \text{ or } A0' B0' = A0 \text{ xnor } B0$$

$$G = F \text{ and } (A1 B1 \text{ or } A1' B1') = F \text{ and } (A1 \text{ xnor } B1)$$



$G = 1$  when  $A1 A0 = B1 B0$ , equality circuit

BR 6/00

8

# Charge Sharing analysis

Worse case occurs when:  
 $C1, C2$  or  $C1, C3$   
precharged low,  $C_n$   
precharged high, and  
during evaluation  $C_n$  is  
supposed to remain high  
(no path to ground but path  
to either  $C2$  or  $C3$ ).

Both  $C2$  &  $C3$  cannot affect  $C_n$  because of  
 $A1, A1'$

BR 6/00

9

## Input Sequence

Need C1, C2 precharged low.

First clock, have  $F=0$  ( $A_0=1$ ,  $B_0=0$ ), and  $A_1=1$ ,  $B_1=1$ . This set  $C_1, C_2 = 0$ .

Second clock, need  $F=1$  ( $A_0=1$ ,  $B_0=1$ ) so we have access to node Cn. Also need access to Node C2 ( $A_1 = 1$ ), but C2 needs to be cutoff from ground ( $B_1=0$ ).


Note: if you just test this circuit using all 16 possible combinations of  $A_1, B_1, A_0, B_0$  will not necessarily see charge sharing problem. Charge storage makes this a sequential circuit!!! (behavior depends on previous input sequence!!!)

BR 6/0010

Charge Sharing Problem. Input sequence.

1<sup>st</sup> clock: A1A0= 11, B1B0: 10, 2<sup>nd</sup> clock: A1A0:11, B1B0:01

 G output should be 0, but is 1. Internal node GG drops.




Pre = 4\*Lmin width, High Skew inverter 4/1, no GEO parameters.

BR 6/00

11

 With GEO params, charge sharing not apparent on output.




Pre = 4\*Lmin width, High Skew inverter 4/1, with GEO parameters. GEO parameters with source/drain sharing reduced node capacitance so output only about 0.3 v.

BR 6/00

12

 Use extra precharge transistor to eliminate charge sharing.




Pre =  $4 * L_{min}$  width, High Skew inverter 4/1, no GEO parameters.

With extra pre-charge transistor to eliminate charge sharing.

BR 6/00

13
 
### Effect of Precharge Width on Charge sharing




No extra precharge transistor, Pre width at  $8 * L_{min}$ , high skew output inverter, No GEO. Output high enough to cause concern.

BR 6/00

14
 
## Effect of Inverter skew on output value



No extra precharge transistor, Pre width at  $8 * L_{min}$ , normal skew inverter, No GEO. Normal skew inverter has higher threshold, so input not as susceptible to charge sharing.

BR 6/00

15

## Delays

	Times in ps
No Geo	Tplh
Inv 4/1, Pre= $4 * L_{min}$	461
Inv 4/1 Pre= $4 * L_{min}$ , extra Pre tran	474
Inv 4/1, Pre= $8 * L_{min}$	500
Inv 2/1, Pre= $8 * L_{min}$	524
With Geo	
Inv 4/1, Pre= $4 * L_{min}$	447

BR 6/00

16



## Observations

- Larger precharge transistors adds extra source diffusion capacitance, which offsets charge sharing
- High skew inverter speeds circuit, but lower input threshold makes it more susceptible to threshold sharing.
- Extra precharge transistor slows circuit because more internal node capacitance.
- GEO parameters reduced internal node capacitance so charge sharing not visible on output.