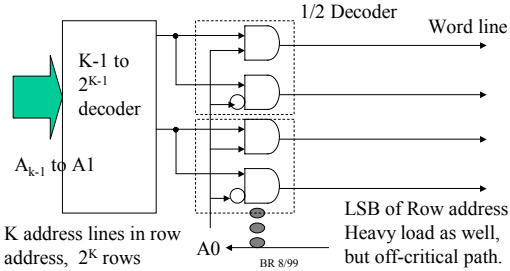


## Word Line Driver

Last stage of row decoding typically decodes only 1-address line (1/2 decoder) because the final stage must be sized to drive the word line load (word-line driver).




## Mitsubishi 4 Mbit SRAM


- 4Mb x 1,  $2^{22}$  bits, 22 address lines
- A single square array would be  $2^{11}$  rows x  $2^{11}$  columns, each word line would have 2048 RAM cell loads!!
- Use hierarchical decoding to break large array into smaller arrays
- Use 32 blocks
  - Each block is 1024 rows x 128 columns = 128Kb
  - $128\text{Kb} \times 32 = 2^{17} \times 2^5 = 2^{22} = 4\text{ Mb}$ .
  - 7 bits for column decode (128 columns). Remaining bits (15) for block (5), row decode (10).

BR 8/99

## Decoding Scheme

 

## Decoding Scheme, another View

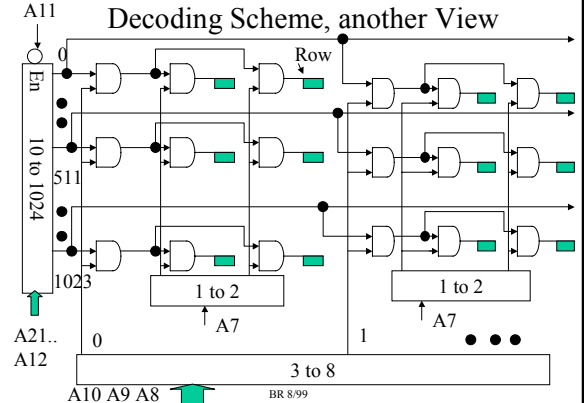

## Loading


- On 10 to 1024 decoder outputs
  - 8 loads (16 blocks divided into 8 groups of 2)
- On 3 to 8 decoder outputs
  - 1024 loads
- On 2 to 1 decoder outputs
  - 1024 loads

Want to equalize delay paths:

complex decode + light load = small decode + large load  
 10 to 1024      8 loads      =      3 to 8      1024

BR 8/99

## Critical Decode Path

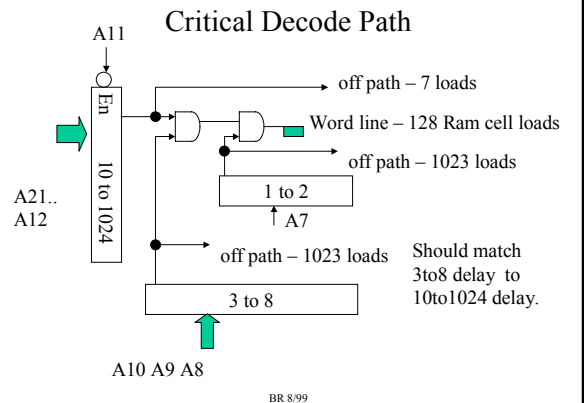


## Cypress 1 Mb Dual Port RAM

- Arranged 64K x 16
- Array split into 32 blocks, each 512 rows by 64 bits (4 words of 16)
  - 16 sense amps per block, 1 sense amp per bit shared among 4 words
  - $32 \text{ blocks} \times 512 \text{ rows} \times 64 \text{ bits} = 2^5 \times 2^9 \times 2^6 = 2^{20}$ .

Plane(1) | Max WL(9) | Min WL(2) | Row Grp(2) | Col(2)

A15 | A14..A6 | A5A4 | A3 A2 | A1..A0

BR 8/99

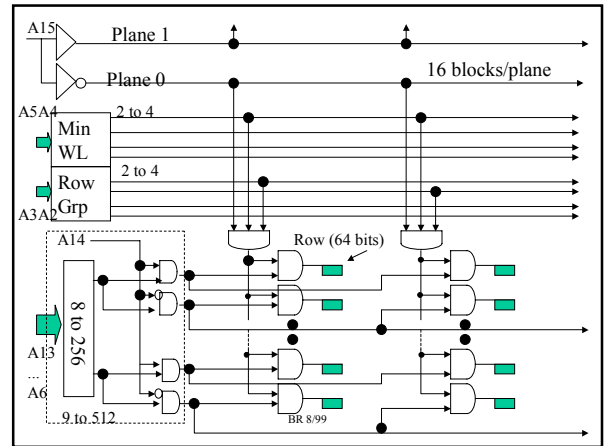

## Loading

- on 8 to 256 decoder output (2 loads)
- on A14 (512 loads)
- on 9 to 512 decoder outputs (16 loads)
- on 4 to 16 decoder (combined Min WL + Row Grp)
  - 512 loads
- On final wordline driver output (64 SRAM loads)

Delays:

Want Dx = 8 to 256 decoder = A14 (512 loads)


Want Dy = 4 to 16 decode (512 loads) = 9 to 512 (64 SRAM bit loads)

BR 8/99


## Misc Comments

- The plane bit is not involved in the Major Word line decoding.
  - Both Major Row decoders active but still only one final word line is active
- Physical layout had Row Group and Min WL lines running down the center of the chip with planes on left/right side

BR 8/99

 

BR 8/99

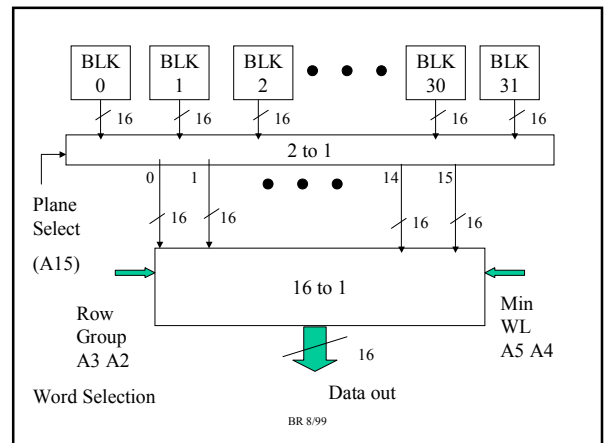


BR 8/99
 
## Fast Decoders


Need Fast, Wide Decoders for Row Decode.

Because of large number of inputs, use a NOR form with a static pullup or precharged pullup.



BR 8/99


## Fast Decoders (cont)

 

Precharge can be generated from clock or address transition detection logic.


BR 8/99

## Power Decoded NOR

 

A NOR gate version that saves power.

BR 8/99

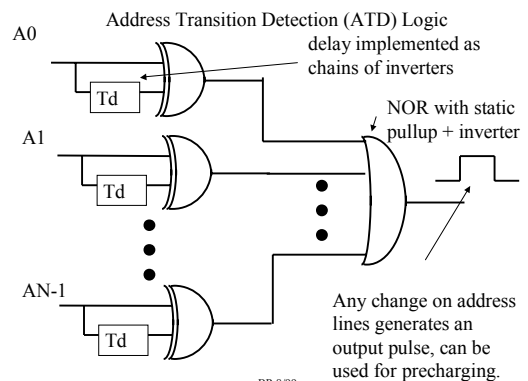

BR 8/99