

## Simulation #2: Bus Operation

- This lecture will discuss some topics that will be useful for performing Simulation #2
  - VHDL Variables
  - Modeling of Finite State Machines
  - Modeling of In/Out Ports
  - Bus Operation
- Also see the link to Simulation #2 on the WWW page

1/22/2003

BR

1

## VHDL Variables

- VHDL variables come in two varieties: global and local
- Local variables can only be declared in processes, procedures, and functions

```
process (clk, r)
variable a: integer := 0;
begin
    .....
    a := a + 1;
    .....
end;
```

- Variable assignments use the “:=” operator
- Variable assignments take place immediately (unlike signal assignments which only place entries on the time queue; the time queue entries are not processed until the process is suspended).

1/22/2003

BR

2

## VHDL Variables (continued)

- Local variables are not visible outside of a process
- For a process, the value of a variable is static, i.e., it retains its value between process invocations
- For a procedure or function, the value of the variable is re-initialized each time the procedure or function is called
- A global variable is declared outside of a process using the ‘shared’ keyword. Will discuss global variables in more detail later.

```
architecture a of myentity is
shared variable a: integer := 0;
process (clk, r)
begin
    .....
    a := a + 1;
    .....
end;
```

1/22/2003


BR

3
 
## Finite State Machines

A Mealy-type FSM is shown below. In a Mealy-type FSM, the outputs are a function of both the present state and the current inputs.

One way to model this to use a separate processes for the state registers and combinational logic.




1/22/2003

BR

4

## FSM Example

 

1/22/2003

BR

5

## Entity

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

-- MEALY FSM machine
-- pstate A=0 A=1
-----
-- S0 | ST0 / 0 ST3/1 == entries are nextstate/outputZ
-- S1 | ST1 / 1 ST0/0 == entries are nextstate/outputZ
-- S2 | ST2 / 0 ST1/1 == entries are nextstate/outputZ
-- S3 | ST2 / 0 ST1/0 == entries are nextstate/outputZ
--
entity mealy_fsm is
port (
    a, clk: in std_logic;
    z: out std_logic
);
end mealy_fsm;
```

1/22/2003

BR

6

## Architecture

```
architecture behv of mealy_fm is
-- enumerated type for state definitions
type mystate is (ST0,ST1,ST2,ST3);
signal p_state, n_state : mystate;
begin
  seq_part: process(clk)
  begin
    if (clk = '0' and clk'event) then
      p_state <= n_state;
    end if;
  end process seq_part;
-- note that this process triggers only on changes to any of its inputs,
-- namely 'p_state' and 'a'
  comb_part: process (p_state,a)
  begin
    -- assign default output values
    z <= '0'; -- default is output
    n_state <= p_state; -- stay in same state by default
    case p_state is
      when st0 => if (A = '1') then z <= '1'; n_state <= st3; end if;
      when st1 => if (A = '1') then n_state <= st0;
        else z <= '1'; end if;
      when st2 => if (A = '1') then z <= '1'; n_state <= st1; end if;
      when st3 => if (A = '0') then n_state <= st2;
        else n_state <= st1; end if;
    end case;
  end process comb_part;
end behv;
BR
```

falling edge state register

7

## Keep Track of #Clock Cycles in State ST0: Try #1

```
comb_part: process (p_state,a)
variable st0_count: integer := 0;
begin
-- assign default output values
z <= '0'; -- default is output
n_state <= p_state; -- stay in same state by default
case p_state is
  when st0 => if (A = '1') then z <= '1'; n_state <= st3; end if;
    st0_count := st0_count + 1;
  when st1 => if (A = '1') then n_state <= st0;
    else z <= '1'; end if;
  when st2 => if (A = '1') then z <= '1'; n_state <= st1; end if;
  when st3 => if (A = '0') then n_state <= st2;
    else n_state <= st1; end if;
end case;
end process comb_part;
```

Wrong: st0\_count incremented anytime 'A' changes while in state ST0

1/22/2003

BR

8

## Keep Track of #Clock Cycles in State ST0: Try #2

```
comb_part: process (p_state,a)
variable st0_count: integer := 0;
begin
-- assign default output values
z <= '0'; -- default is output
n_state <= p_state; -- stay in same state by default
case p_state is
  when st0 => if (A = '1') then z <= '1'; n_state <= st3; end if;
    if (pstate'event) then
      st0_count := st0_count + 1;
    end if;
  when st1 => if (A = '1') then n_state <= st0;
    else z <= '1'; end if;
  .....
end process;
```

Wrong: st0\_count incremented anytime we enter ST0 from a different state (pstate changes) but does not count clock cycles that A=0 and we are in state ST0.

1/22/2003

BR

9

## Keep Track of #Clock Cycles in State ST0: Try #3

```
comb_part: process (p_state,a,clk)
variable st0_count: integer := 0;
begin
-- assign default output values
z <= '0'; -- default is output
n_state <= p_state; -- stay in same state by default
case p_state is
  when st0 => if (A = '1') then z <= '1'; n_state <= st3; end if;
    if (clk'event and clk = '1') then
      st0_count := st0_count + 1;
    end if;
  when st1 => if (A = '1') then n_state <= st0;
    else z <= '1'; end if;
  .....
end process;
```

Will work; clk must be added to sensitivity list, and the check occurring on rising edge will cause the variable to be updated in the middle of the clock cycle. If you check the falling edge of clk, then the variable is updated at the end of the clock cycle. The process is executed twice every clock cycle (once for each change in clk).

1/22/2003

BR

10

## Keep Track of #Clock Cycles in State ST0: Try #4

```
comb_part: process (p_state,transaction,a)
variable st0_count: integer := 0;
begin
-- assign default output values
z <= '0'; -- default is output
n_state <= p_state; -- stay in same state by default
case p_state is
  when st0 => if (A = '1') then z <= '1'; n_state <= st3; end if;
    if (pstate'active) then
      st0_count := st0_count + 1;
    end if;
  when st1 => if (A = '1') then n_state <= st0;
    else z <= '1'; end if;
  .....
end process;
```

Will work; 'active returns true anytime a transaction (an assignment) is made to pstate, which happens every clock cycle via the seq\_part process. Added pstate'transaction to sensitivity list because 'transaction returns a signal that toggles for each transaction. This process executes only once per clock cycle, is more efficient than previous solution.

1/22/2003

BR

11

## Count # of state transitions from ST0 to ST3 Try #1 (some code deleted for brevity) – put counter in ST0

```
comb_part: process (p_state,a)
-- 'counter' will count transitions from 'st0' to 'st3'
variable counter: integer := 0;
begin
-- assign default output values
z <= '0'; -- default is output
n_state <= p_state; -- stay in same state by default
case p_state is
  when st0 => if (A = '1') then z <= '1'; n_state <= st3;
    counter := counter + 1;
  end if;
  when st1 => if (A = '1') then n_state <= st0;
    else z <= '1'; end if;
  .....
end process;
```

Will not work if A goes from '0' to '1' and back to '0' while in state ST0. Will not transition to ST3, yet counter is incremented.

1/22/2003

BR

12

### Count # of state transitions from ST0 to ST3

Try again...put counter in State ST3

```
when st3 =>
  counter := counter + 1;
```

Wrong, will increment anytime we are in ST3 and process triggers – not that a change in ‘A’ can cause the process to trigger.

```
when st3 =>
  if (p_state'event) then
    counter := counter + 1;
  end if;
```

This will work because counter only incremented on change to *p\_state* and only way to get to ST3 is from ST0.

### Count # of state transitions from ST0 to ST3

What if ASM chart has more than one way to get to ST3? (i.e., the ASM chart included a transition from ST2 to ST3, but only wanted to count transitions from ST0 to ST3).

```
when st3 =>
  -- the signal attribute 'last_value' returns the last value of the
  -- signal; it is useful here.
  if (p_state'event and (p_state'last_value = st0)) then
    counter := counter + 1;
  end if;
```

The attribute ‘last\_value’ gives the previous value of the signal – can use it here to see if previous state was ST0.

### Port Types

- VHDL port types can be *in*, *out*, *inout*, *buffer*
  - in* intended for input-only ports. Cannot assign values to ports of type *in*.
  - out* intended for output-only port. Cannot read the value of ports of type *out*.
  - inout* intended for bidirectional ports
  - buffer* type is like an *out* port but can be read from
- Do not use *buffer* ports. Problems are:
  - a *buffer* port can only have one driver on it
  - a *buffer* port must be connected to another port of type *buffer*, which means *buffer* ports propagate through hierarchy
- If you need to read a value from an *out* port, use the *driving\_value* attribute
  - Will return the driving value of the port, can be used to read the driving value of a port of type *out*.

### Modeling a bidirectional port

- A bidirectional port means that sometimes your model is providing the drive, and that sometimes another component is providing the drive for the signal
- Use an *inout* type for the port type
  - y*: *inout* *std\_logic* ;
- Internal to your model, keep track of when your model is supposed to be providing the drive. I usually declare two internal signals
  - y\_out* -- internal signal that model will drive
  - dir* -- ‘direction’ signal that tells me if the model is supposed to be driving or not


### Modeling a bidirectional port

```
entity example is
  port (clk: std_logic;
        y: inout std_logic);
end example;

architecture a of example is
  signal dir: std_logic := '0'; -- '0' reading, '1' driving
  signal y_out: std_logic := 'Z';
begin
  y <= y_out when (dir = '1') else 'Z';
  ....
  process (clk)
  ... some process
  when STATE_A: dir <= '1'; y_out <= '1'; -- drive some value
  ....
  when STATE_K: dir <= '0'; --- let some other model drive this signal
  ....
  when STATE_N: if (y = '1') then.... -- can read an 'inout' port
                -- will read the resolved value!!
```

‘Z’ value is important – this lets external component override this signal

### Sim #2 *bbusy* signal

 

*bbusy* is a ‘bus busy’ signal. When a CPU owns the bus, it should drive the *bbusy* line to ‘0’. When a CPU does not own the bus, it should have the line released (driving a ‘Z’). When a CPU is granted the bus, it must watch the *bbusy* line to see if the bus is free (value of ‘H’). If the bus is free and the CPU has been granted the bus, then the CPU can claim the bus by driving *bbusy* low. Note that *bbusy* is a *bidirectional* signal!!